

Unit 2.1 - Binary Numbers

Binary digit: $b_n | b_{n-1} | b_{n-2} | \dots | b_1 | b_0 \Rightarrow \text{value} = \sum_i b_i \cdot 2^i$

Value : $\begin{array}{c|c|c|c|c|c} & b_n & b_{n-1} & b_{n-2} & \dots & b_1 & b_0 \\ \hline & 2^n & 2^{n-1} & 2^{n-2} & & 2^1 & 2^0 \end{array}$

Max value with k bits: $1 + 2 + 4 + \dots + 2^{k-1} = 2^k - 1$

With 8 bits, can represent 256 different binary numbers $\Rightarrow 2^8 = 256$

~~0000 0000
0000 0001
0000 0011
0000 0111
0000 1111
0001 1111
0011 1111
0111 1111
1111 1111~~ \rightarrow reserving last digit on left for negative numbers leaves 127 possible numbers to be used with 8 bits

$$\frac{256-2}{2} = 127$$
Decimal \rightarrow Binary

$$87_{\text{decimal}} = 64 + 16 + 4 + 2 + 1 \Rightarrow \begin{array}{c|c|c|c|c|c|c|c|c} & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\ \hline 0 & 1 & 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ \hline + & 64 & 0 & 16 & 0 & 4 & 2 & 1 & 1 \end{array}$$

\hookrightarrow start with largest factor 2

Base 10

e.g. 789_{10}

$$\begin{array}{r} 789_{10} \\ \downarrow \\ 7 \cdot 10^2 + 8 \cdot 10^1 + 9 \cdot 10^0 \end{array}$$

Unit 2.2 - Binary Addition

2020-09-07

$$\begin{array}{r}
 1 \ 1 \ 1 \\
 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 1 \\
 + 0 \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 \\
 \hline
 0 \ 1 \ 1 \ 1 \ 0 \ 0 \ 0 \ 1
 \end{array}$$

carry the one

Overflow

$$\begin{array}{r}
 1 \ 1 \ 1 \\
 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 1 \\
 + 1 \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 \\
 \hline
 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 1
 \end{array}$$

- overflow bit will be truncated
- ∴ in a computer, cannot do real integer addition

Half Adder

?	?	?	?	?	?	a	?	?
?	?	?	?	?	?	b	?	?
							□ - sum	

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

↳ carry over a must = 0

↳ truth table for chip


Full Adder

?	?	?	?	?	?	?	?	?
?	?	?	?	?	?	b	?	?
							sum	

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

16-Bit Adder

⇒ 15 full adders
with one half adder
for right most bit

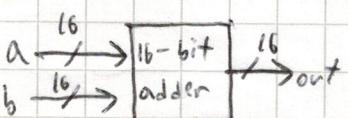

Unit 2.3 - Negative Numbers

2020-04-07

Sign Bit

0000	0	$\rightarrow 0$
0001	1	$\rightarrow 1$
0010	2	$\rightarrow 2$
0011	3	$\rightarrow 3$
0100	4	$\rightarrow 4$
0101	5	$\rightarrow 5$
0110	6	$\rightarrow 6$
0111	7	$\rightarrow 7$
1000	-0	$\rightarrow -8 \text{ (8)}$
1001	-1	$\rightarrow -7 \text{ (9)}$
1010	-2	$\rightarrow -6 \text{ (10)}$
1011	-3	$\rightarrow -5 \text{ (11)}$
1100	-4	$\rightarrow -4 \text{ (12)}$
1101	-5	$\rightarrow -3 \text{ (13)}$
1110	-6	$\rightarrow -2 \text{ (14)}$
1111	-7	$\rightarrow -1 \text{ (15)}$

Two's Complement

- represent negative number $-x$ using the positive number: $2^n - x$

- positive numbers in range $0 \dots 2^{n-1} - 1$

- negative numbers in range $-1 \dots -2^{n-1}$

inelegant

'messy' hardware config.

Addition in 2's Complement

$$\begin{array}{r}
 -2 \\
 + -3 \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 14 \\
 + 13 \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 1110 \\
 + 1101 \\
 \hline
 11011
 \end{array}
 \rightarrow
 \begin{array}{l}
 11011 = 27_{\text{ten}} \\
 1011 = 11_{\text{ten}} \\
 11 \Rightarrow \boxed{-5} \text{ in 2's complement, correct answer}
 \end{array}$$

Representation is modulo 2^n

Addition is modulo 2^n

Unit 2.3 - Negative Numbers (continued)

Computing $-x$ → solving this allows us to subtract: $y - x = y + (-x)$
 \hookrightarrow addition is solved

input: x

output: $-x$ (in 2's complement)

idea: $2^n - x = 1 + (2^n - 1) - x$



$$2^n - 1 = \boxed{111 \dots 1}_2$$

~~is just flipping each bit~~

e.g. input: 4 (0100)

output: -4 → 2's complement = 12₁₀, 1100

$(2^n - 1) - x$ is just flipping each bit

e.g. $\begin{array}{r} 1111 \\ - 1010 \\ \hline 0101 \end{array}$ → then add one

$$\begin{array}{r} 1111 \\ - 0100 \\ \hline 1011 \end{array} \quad \begin{array}{c} \nearrow \\ + 1 \end{array} \quad \begin{array}{r} 1100 \\ \hline \end{array}$$

→ to add 1, start at right most bit, flip
 1s to 0s and stop when you flip a 0
 to 1

★ Using two's complement and method for addition, can have a
 method for subtraction



to increment binary number by 1:

Half Adder ($a = \text{in}[0]$, $b = \text{True}$, $\text{out} = \text{out}[0]$, $\text{carry} = c_1$) → Pipe carry forward.


Full Adder ($a = \text{in}[1]$, $b = \text{false}$, $c = c_1$, $\text{out} = \text{out}[1]$, $\text{carry} = c_2$)

Full Adder ($a = \text{in}[1]$, $b = \text{false}$, $c = c_{15}$, $\text{out} = \text{out}[15]$, $\text{carry} = c_{16}$)

\hookrightarrow first b input is true, subsequent b inputs are false

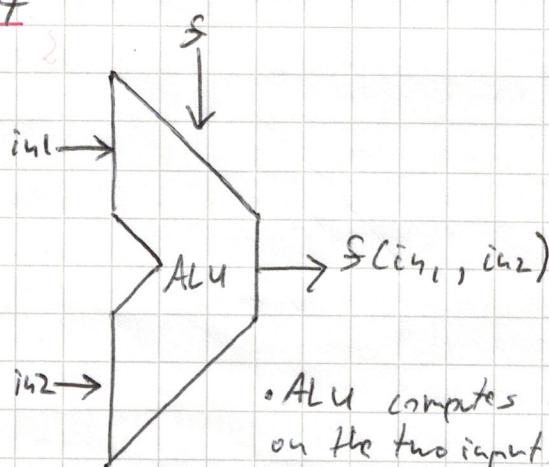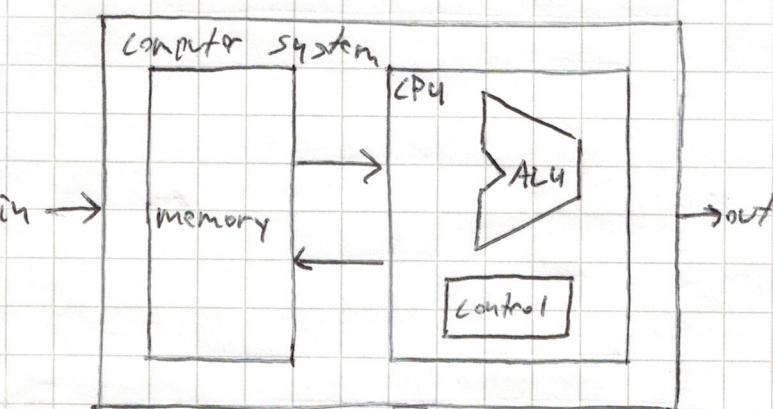Unit 2.4 - Arithmetic Logic UnitVon Neumann Architecture

- ALU computes a function f on the two inputs and outputs the result
- f is one of a family of predefined arithmetic and logical functions
- the operations an ALU can do is a hardware/software trade off

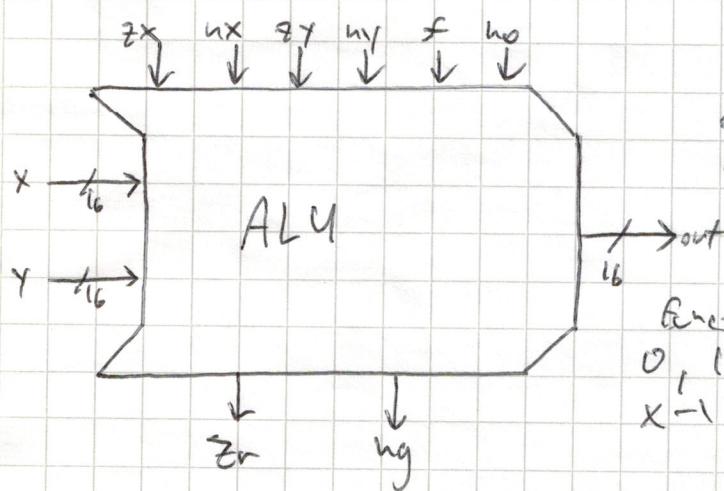The Hack ALU

- Inputs: two 16-bit 2's complement values
 Output: one 16-bit 2's complement value
 • function to compute set by 6 1-bit control inputs
 • Also outputs two 1-bit control outputs

Functions:
 $0, 1, -1, x, y, !x, !y, -x, -y, x+1, y+1,$
 $x-1, y-1, x+y, x-y, y-x, x\&y, x\|y$

Hack ALU operation

zx	nx	zy	ny	f	no	out
if zx then $x=0$	if nx then $x=!x$	if zy then $y=0$	if ny then $y=!y$	if F then $out=x+y$ else $out=x\&y$	if no then $out=\text{!}out$	$out(x, y) =$

Subsequent operations are done on processed input f

Control output 1 — Z_r and ng

if $out = 0$ then $Z_r = 1$, else $Z_r = 0$ } comes into play in next building
 if $out < 0$ then $ng = 1$, else $ng = 0$ } complete architecture